G. Lohninger

A 15 GHz GaAs-FET Buffered Oscillator

A buffered stable oscillator has been developed using a parallel feedback circuit, two CFY35GaAs- field effect transistors and a dielectric resonator. In addition a spacer for a high resonator quality-factor is added. The design goals for this oscillator are high output power > 10dBm, low phase noise < -95 dBc/Hz at 100 kHz offset and high stability versus load impedance variations and versus temperature. The emphasis has been also on small size and high reliability (Fig.1/ 2).



Fig. 1 / 2 The buffered oscillator circuit on a teflon board (er= 2.4, h= 0.38mm and t=17 μ 5m Cu) consists of several surface mounted devices and plated thru holes. The resistors and capacitors used have dimensions of 2mm x 1.27mm. The CFY35 transistors are housed in a MW4 package.

By turning on the DC-bias, the oscillator starts up from noise to a power level, that depends on the load impedance i.e. the input reflection coefficient of the buffer amplifier circuit. That is why the capacitance 12 pF can be used to optimize the tuning range and the output power of the parallel feedback oscillator circuit.

A microstrip tuning stub and the capacitor 22pF at the output of the buffer amplifier provide high gain values.

Table 1 and Figure 3 / 4 show the small signal simulation of the oscillator. The output MAG S11 can be maximized up to 40 by the variation of the microstrip lines. Though Microwave Harmonica 6.0 offers a DR-model, a RLC-circuit and two ideal transformer (trf) simplify the simulation.



Table 1 and Fig. 3 / 4 Small signal analysis of the oscillator without buffer amplifier.

The two circuits - oscillator and buffer amplifier - are working in a saturation current mode. The operating current without oscillation (I_{DSS} , $U_{G}=0$) will be reduced by self biasing effects after start up.

SIEMENS

Discrete & RF Semiconductors

Table 2 shows the typical characteristics of the circuit housed in a metal cavity. Please pay attention to cavity oscillation effects. These phenomenas can be avoided by the use of absorber material or optimized cavity dimensions.

14.5 to 15.3 GHz
- 40 °C to + 120 °C
12 dBm
±1 dB
50 Ohms
- 2MHz to + 7MHz
3 MHz / V
< - 95 dBc/Hz
+ 5 V
37 mA

 Table 2 Typical characteristics of the buffered oscillator.

<u>References</u>

- 1) R. Soares: GaAs-MesFET Circuit Design, Artech House, Inc., 1988.
- 2) G.Gonzales: Microwave Transistor amplifiers Analysis and Design, Prentice-Hall, Inc., 1984.
- 3) Application Note No.002: Silicon Bipolar-Dielectric Resonator Oscillator (DRO) at 10 GHz
- 4) G. Lohninger, "Oszillatordesign in der Hochfrequenztechnik," Elektronik, Heft 03/95.

G.Lohninger HL EH PD1 3.1.95

Published by Siemens AGBereichBauelemente,Vertrieb, Produkt-Information,Balanstraße 73, D-81541München
© Siemens AG 1994. All Rights Reserved
As far as patents or other rights of third parties are concerned, liability is only assumed for components per se, not for applications, processes and circuits implemented within components or assemblies.
The information describes the type of component and shall not be considered as assured characteristics.
Terms of delivery and rights to change design reserved.
For questions on technology, delivery and prices please contact the Offices of Semiconductor Group in Germany or the Siemens Companies and Representatives world-wide (see address list).
Due to technical requirements components may contain dangerous substances. For information on the type in question please contact your nearest Siemens Office, Semiconductor Group.
Siemens AG is an approved CECC manufacturer.